

# Exercise 05: Feedback Analysis and simulation

## <Advanced Analogue Building Blocks>



Kirchhoff-Institute for Physics, Uni-Heidelberg



Zhenxiong Yuan

2017.06.10



# Contents



- A short review of feedback loop-gain
- Return ratio analysis for feedback loop
- Exercise:
  - Analysis of a capacitive-feedback amplifier
  - “stb” simulation in virtuoso




# Overview of feedback



- Basic diagram of negative feedback
  - Loop-gain ( $T$ ), closed-loop gain ( $A$ ), ...
  - Stability: phase margin, gain margin,...

$$\frac{S_o}{S_i} = A = \frac{a}{1 + af}$$

$$T = af$$

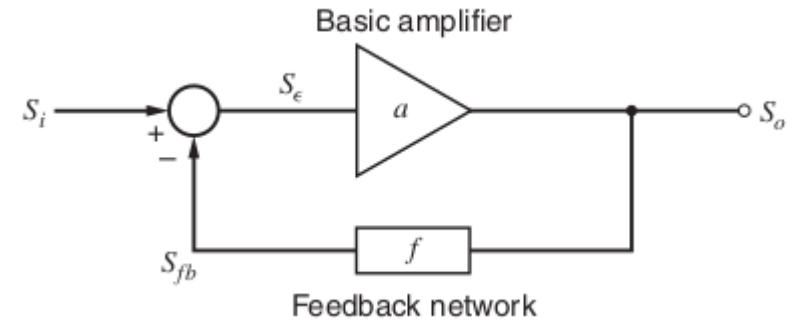

- it's not straight-forward to get the feedback diagram
  - Load effect from the feedback loop
  - Forward feedback by the feedback loop, ...
- How to analysis a feedback loop?
  - Two-port network analysis
  - **Return ratio** methods
- Simulation: “**stb**” in Spectre




# Return ratio



- Procedure for analysis **loop-gain** using return-ratio method
  - Set all independent sources to zero
  - Disconnect the dependent source from the rest of the circuit, which introduces a break in the feedback loop
  - On the side of the break that is not connected to the dependent source, connect an independent test source  $\mathbf{S}_t$  of the same sign and type as the dependent source
  - Find the return signal  $\mathbf{S}_r$  generated by the dependent source.

$$T = -\frac{S_r}{S_t}$$

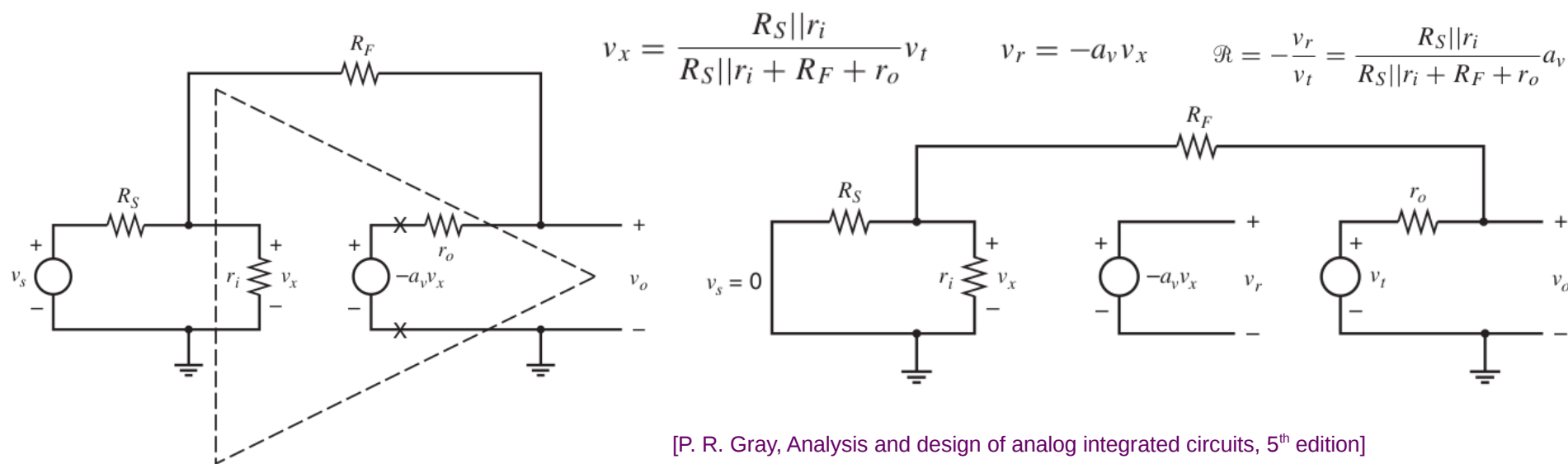




# Return ratio



- Analysis of **closed-loop gain** using return ratio method

$$A(s) = A_{\infty} \frac{T(s)}{1+T(s)} + \frac{d(s)}{1+T(s)}$$

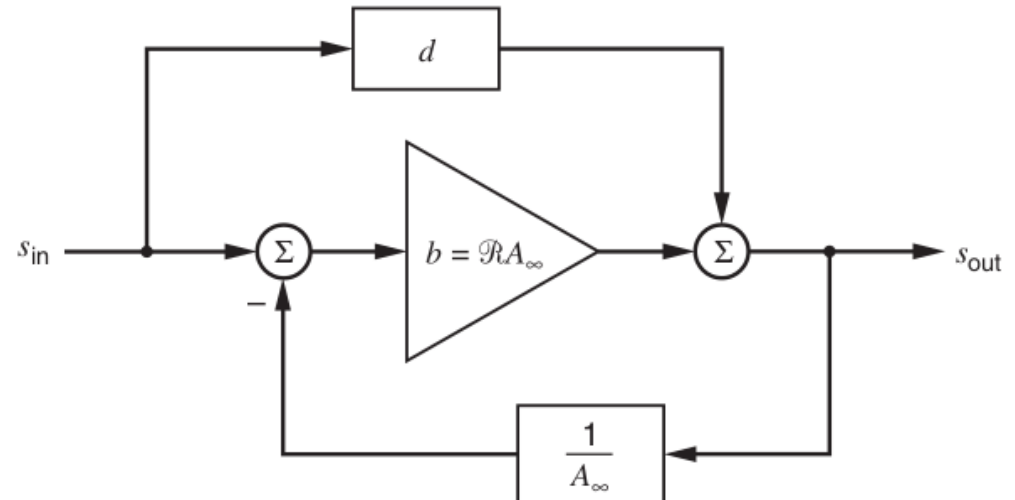- Very tedious to get this formula
  - $A_{oo}$ : ideal closed-loop gain (idea amplifier, or set the coefficient of a dependent source to be infinity, and calculate the  $V_o/V_i$ )
  - $d(s)$ : gain of direct feed-through (set the coefficient of a dependent source to be zero, and calculate the  $V_o/V_i$ )





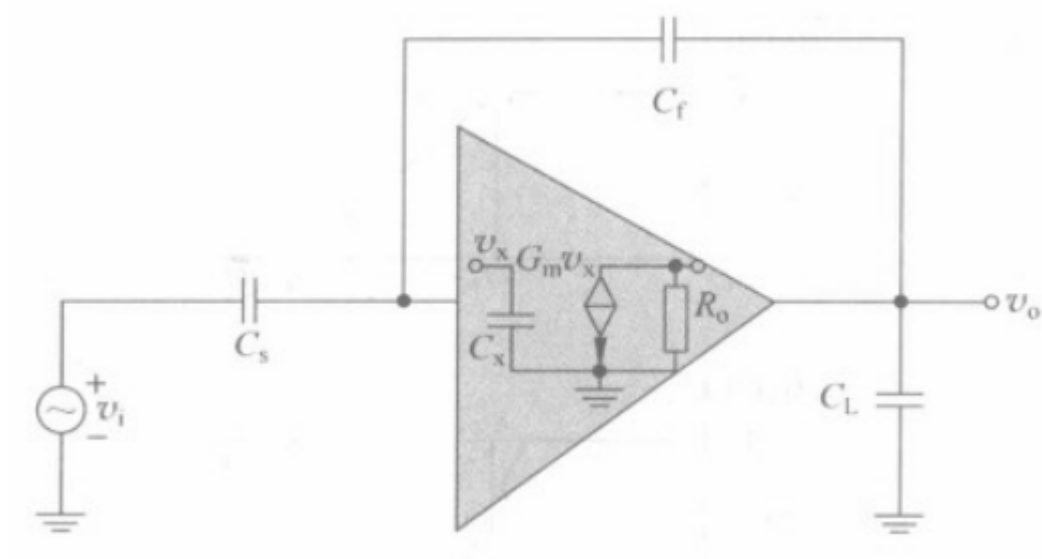
# Exercise: analysis



- Capacitive-feedback amplifier with OTA used
  - Loop-gain
  - Closed-loop gain






# Exercise: analysis loop-gain



- Derive Loop-gain expression  $T(s)$
- Draw the bode-plot, calculate the bandwidth, unity gain-bandwidth
- Estimate the phase margin



# Exercise: analysis loop-gain

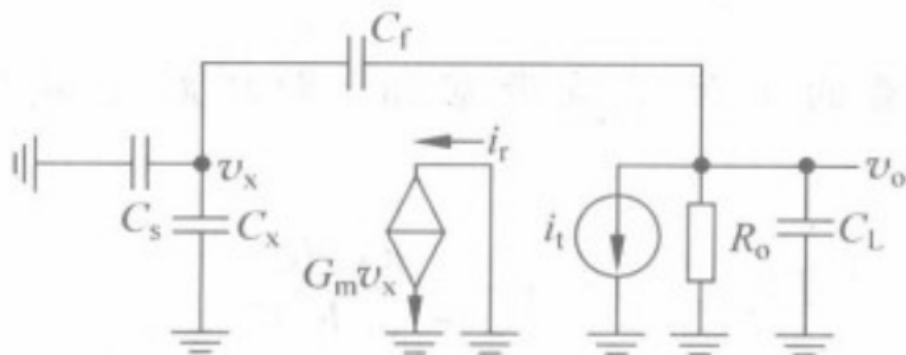

$$v_x = \frac{C_f}{C_f + C_s + C_x} v_o = \beta v_o$$

$$\beta = \frac{C_f}{C_f + C_s + C_x} \quad \text{Feedback ratio}$$



$$v_o = -i_t \left( R_o \parallel \frac{1}{sC_{L,tot}} \right)$$

$$C_{L,tot} = C_L + (1 - \beta) C_f \quad \text{Loading effect of feedback loop}$$

$$i_r = -i_t \left( R_o \parallel \frac{1}{sC_{L,tot}} \right) G_m \beta$$

$$T(s) = -\frac{i_r}{i_t} = \frac{\beta G_m R_o}{1 + sR_o C_{L,tot}}$$
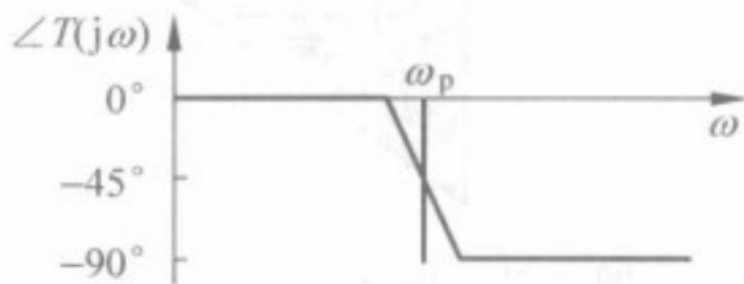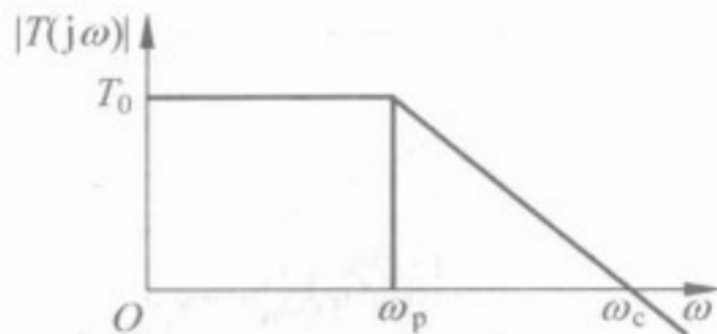
$$T_0 = \beta G_m R_o, \omega_p = \frac{1}{R_o C_{L,tot}}, \omega_c = T_0 \omega_p, PM \approx 90$$








# Exercise: analysis closed-loop gain




- Calculate the full expression of  $d(s)$  and  $A_{oo}$
- Simplify  $d(s)$  at frequency much higher than bandwidth of  $T(s)$
- Simplify  $d(s)$  at low frequency and calculate the static gain-error



# Exercise: analysis closed-loop gain

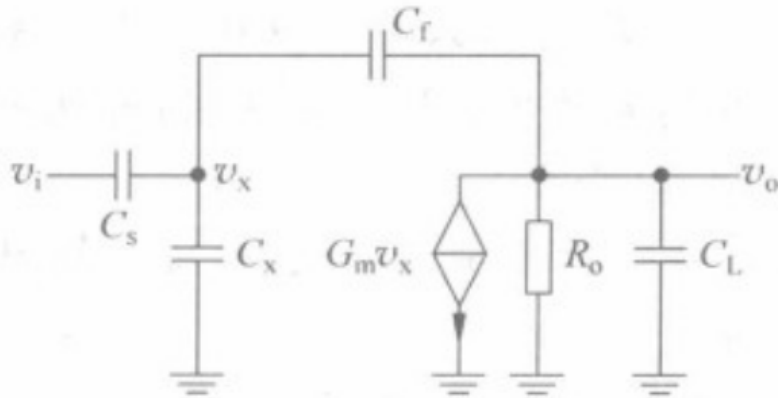

Small signal circuit

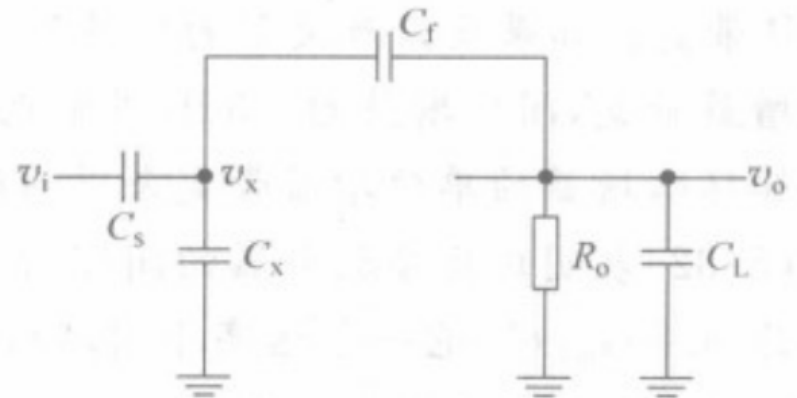

Small signal circuit for calculating  $d(s)$

1. In the small signal circuit, set  $G_m$  to be infinity to calculate the  $A_{\infty}$   $A_{\infty} = -\frac{C_s}{C_f}$
2. In the small signal circuit, set  $G_m$  to be 0 to calculate the  $d(s)$   $d = \frac{(R_o \parallel \frac{1}{sC_L} + \frac{1}{sC_f}) \parallel \frac{1}{sC_x}}{(R_o \parallel \frac{1}{sC_L} + \frac{1}{sC_f}) \parallel \frac{1}{sC_x} + \frac{1}{sC_s}} \frac{R_o \parallel \frac{1}{sC_L}}{R_o \parallel \frac{1}{sC_L} + \frac{1}{sC_f}}$

High frequency:

$$d \approx \frac{C_s C_f}{C_f C_L + (C_x + C_s)(C_f + C_L)}$$

$$A(s) = -\frac{C_s}{C_f} \frac{1 - \frac{sC_f}{G_m}}{1 + \frac{sC_{L,tot}}{\beta G_m}}$$

Zero in right half plan?

-3dB bandwidth?

low frequency:

$$d \approx 0 \quad A_0 = -\frac{C_s}{C_f} \frac{T_0}{1 + T_0}$$

Static gain error:

$$\varepsilon = \frac{A_{\infty} - A_0}{A_{\infty}} = \frac{1}{1 + T_0} \approx \frac{1}{T_0}$$



# Exercise: simulation



- The **STB** analysis linearizes the circuit about the DC operating point and computes the loop-gain, gain and phase margins (if the sweep variable is frequency), for a feedback loop and a gain device.
- Refer to the Spectre Simulation Reference for details
- In “Ex05/OTA\_LoopGain”, using the stored states, do simulation. Try to understand the simulation result

Try to understand the results if the simulation go beyond your expectation...  
I am just too lazy to verify it when I prepare the exercise. Haha~